

P.O.S Canonical Form For Truth Table

Kalyan

September 7, 2022

IIT Hyderaba

Contents

Abstract

This manual shows how to use Arduino with 7447 and sevensegment dispaly to represent pos canonical form for

function 'F' in truth table.

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

h.png										
		X	Y	Z	Ta	ble	2.1			
	Input	0	1	0		10010 2.1				
	egment	a	b	С		1	е	f	g	
74	47	a'	b'	c	, d	ľ	e'	f'	g g'	
Table 2.2										
	7447		Α	В	С	I)			
	Arduii	10	2	-	-	-	-			

table 2.3

Software

execute the following program after downloading.

https://github.com/anirudhkalyan/fwc.git

Components 1

Components	Value	Quantity	
Resistor	220Ohm	1	
Arduino	UNO	1	
Seven segment Display		1	
7447	-	1	
Jumper wires	M-M	20	
Breadboard		1	

X,Y,Z are the inputs that we are assigning manually in bread board and by deriving canonical form for F,

$$F = (X+Y+!Z)*(X+!Y+Z)*(!X+Y+!Z)*(!X+!Y+Z)$$
(1)

2 Hardware

Problem 2.1. Now make the connections as per Table 2.1,2.2 and 2.3

conclusion

open in Geany by using github link provided above then compile and execute

2